

# Boolean Expression to its simplest form using K-map

Akana Sai Kumar  
19pa1a0405@vishnu.edu.in  
IITH - Future Wireless Communication-(FWC22032)

## Contents

1 Introduction	1
2 karnaugh-map	1
3 Components	1
4 Truth table for given expression	1
5 Connections and results	1
5.1 Code Link . . . . .	1

## 1 Introduction

K maps are used to Simplify Boolean Expressions the given Expression to solve  $F(X,Y,Z,W)=(0,1,4,5,6,7,8,9,11,15)$

## 2 karnaugh-map

		ZW			
		00	01	11	10
XY	00	1	1	0	0
	01	1	1	1	1
	11	0	0	1	0
	10	1	1	1	0

$$F=X'Z'+Y'Z'+X'Y+XYZ$$

## 3 Components

Component	value	quantity
Resistor	220 ohm	1
Arduino	UNO	1
LED		1
Bread board		1
Jumper wires	M-M	10

Table 1:

## 4 Truth table for given expression

X	Y	Z	W	F
0	0	0	0	1
0	0	0	1	1
0	0	1	0	0
0	0	1	1	0
0	1	0	0	1
0	1	0	1	1
0	1	1	0	1
0	1	1	1	1
1	0	0	0	1
1	0	0	1	1
1	0	1	0	0
1	0	1	1	1
1	1	0	0	0
1	1	0	1	0
1	1	1	0	0
1	1	1	1	1

Table 2:

## 5 Connections and results

Also make connections to arduino UNO ,led and inputs based on table3.

Arduino UNO	2	3	4	5	8	gnd
Input	X	Y	Z	W		
led					+	-

Table 3:

Sample input	X	Y	Z	W	LED
1	0	0	0	0	ON
2	0	0	1	0	OFF

Table 4:

### 5.1 Code Link

<https://github.com/19pa1a0405/sai1729/blob/main/assign/codes/code1.txt>